

Electricity (Year 4)

Prior Learning

Year 3: Light

- Light travels to Earth from the Sun and other stars but can also be created by Electricity

Year 3 – Forces including magnets

- Lots of metals are magnetic. The ones that are, such as Iron, Nickel or Copper are good conductors of electricity.

Key Vocabulary

Function: Work or operate in a particular way

Cause and Effect:
Something happening because a different thing prompted it to happen

Conduct: Transmit (a form of energy such as heat or electricity) by conduction.

Insulate: Prevent energy from passing through

Complete Circuit: A complete electrical network with a closed loop

Material: the matter from which a thing is or can be made


Key Facts

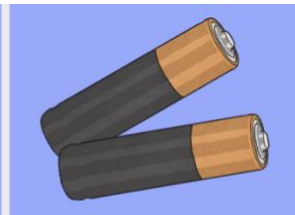- 1) Appliances, like a toaster, run on electricity. Without electricity a lot of everyday objects wouldn't work, i.e. mobile phones, TV's, computers
- 2) A circuit needs to be complete for the electricity to flow through it and make things light up, heat up, etc
- 3) Switches, like a light switch or doorbell, can break or complete a circuit and allow electricity to flow
- 4) Conductors transmit electricity – some metals make good conductors
- 5) Insulators protect items – wires are protected by a plastic material
- 6) Electricity is extremely dangerous and should always be used safely




Images and Icons



Mains electricity: which is an alternating current (AC).



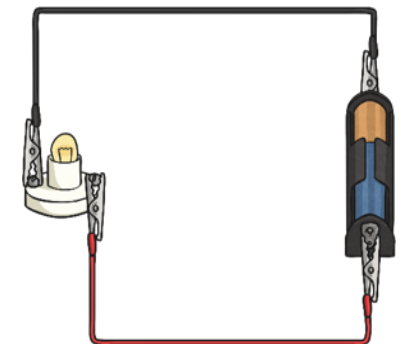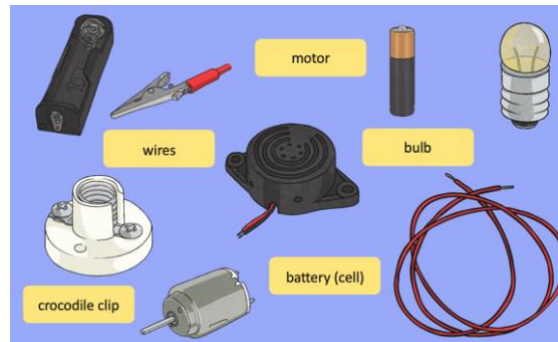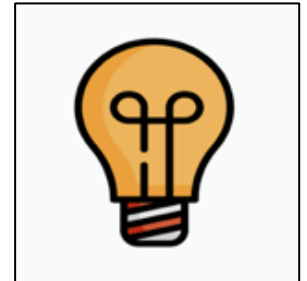Batteries: which generate a direct current (DC).



Electricity (Year 6)

Prior Learning

Year 4: Electricity

- Electrical Conductors are materials that electricity can easily pass through, like copper, iron and gold.
- Electrical insulators don't allow electricity to flow through them, like rubber, plastic and wood
- Components in a circuit could involve a bulb, battery, cell, wires, switch or buzzer.

Key Vocabulary

Function: Work or operate in a particular way

Cause and Effect: Something happening because a different thing prompted it to happen

Component: A part of a larger whole

Dimmer: A device for varying the brightness of a light

Voltage: A unit of measurement showing how much electricity is running in a circuit

Variation: A change or difference

Key Facts

- 1) Electricity can only flow around a complete circuit that has no gaps. There must be wires connected to both the positive and negative end of the power supply.
- 2) Switches can be used to open or close a circuit, affecting the flow of electrons.
- 3) If more bulbs or buzzers are added to a circuit, the power has to be shared so they will be dimmer or quieter
- 4) Shortening wires in a circuit means the electrons have less resistance to flow through
- 5) The voltage and number of cells or batteries will affect the brightness of a bulb.
- 6) Static electricity and lightning are natural forms of electricity.

Images and Icons

